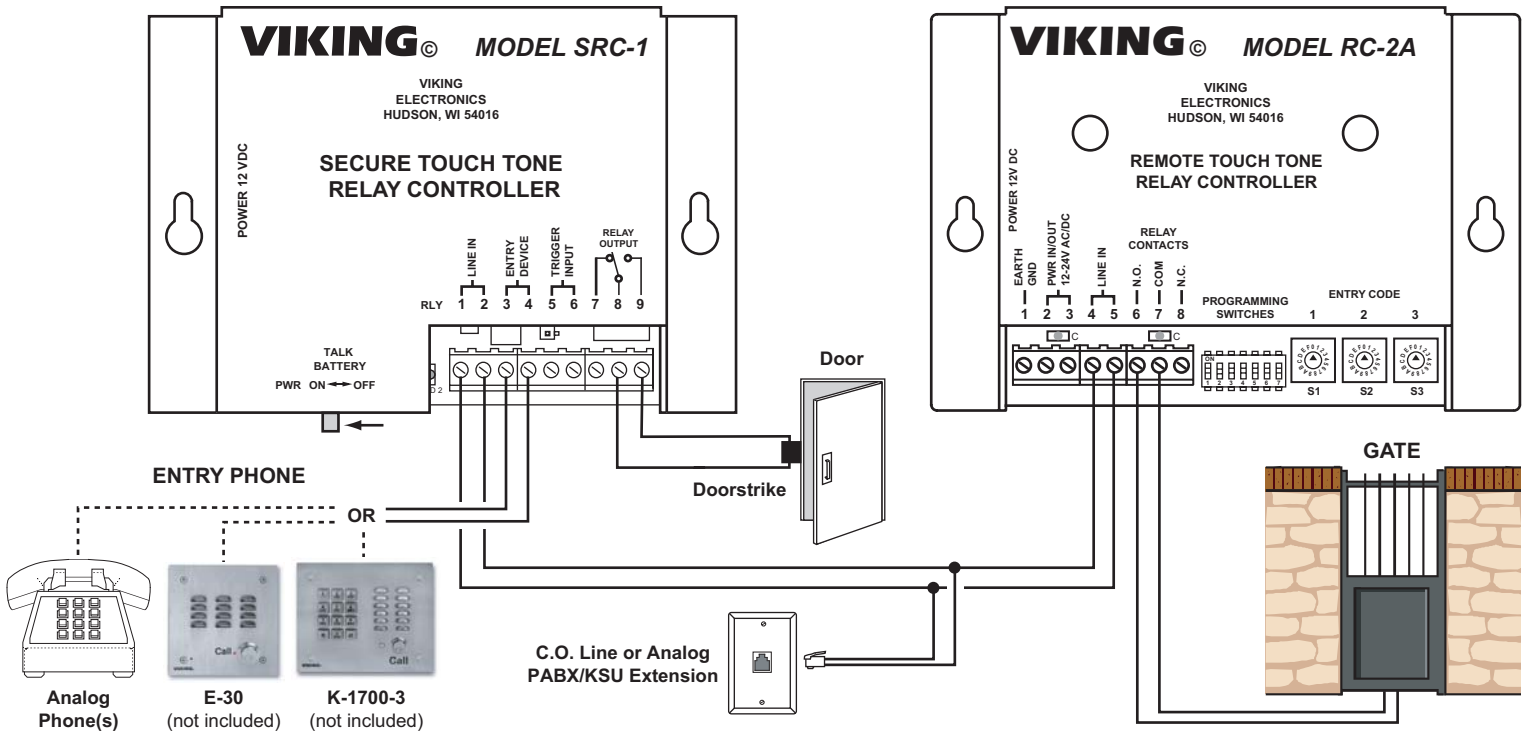


Add a Second Secure Relay to the SRC-1



The SRC-1 provides secure relay control of a single door or gate, meaning the person at the entry phone is not able to operate it. Add an RC-2A to provide a second secure relay to operate a second door or gate.

If the entry phone has no keypad (such as model E-30), the relay command to the SRC-1 can be one or two digits and the command to the RC-2A must be the same length, but cannot match a digit dialed by the entry phone. If the entry phone does have a keypad (such as model K-1700-3), the SRC-1 should be programmed in the "*5" mode (its command is then "***") and the RC-2A command is two digits with the first digit being a "*". If programmed as described, the SRC-1 and RC-2A relays are both secure.